

## Chapter 2 problems 14, 18, 20

14)

This is a voltage divider between the inductor (1 s) and the resistor-capacitor combination (1+1/s).

$$\text{Therefore } \frac{V_o(s)}{V_i(s)} = \frac{s}{s + (1+1/s)} = \frac{s^2}{s^2 + s + 1}$$

18)

The nodal equations for this circuit are written with the following nodes: Vout (which is between the 3 Henry Inductor and the 4 Ohm resistor), Va (which is between the 1 Ohm and 2 Ohm resistors).

Recalling our 210 and 305 knowledge, we write (remember we replace Inductors with L\*s, Capacitors with 1/sC, and Resistors with R)

$$\frac{V_a - v}{1} + \frac{V_a}{1 + 2s} + \frac{V_a - V_{out}}{2 + 3s} = 0$$

$$\frac{V_{out}}{4} + \frac{V_{out} - V_a}{2 + 3s} + \frac{V_{out} - v}{5/s} = 0$$

It should be clear to you how to solve for  $G(s) = V_{out}(s) / v(s)$  from here (you can eliminate Va from the two equations in a variety of ways).

20)

Clearly  $v_1(t) = v_i(t)$  since  $V_+ = V_-$  always.

Doing nodal analysis at  $V_-$ , we can see that

$$\frac{V_i}{200000 + 1/s * 1e-6} + \frac{V_i - V_o}{100000 + 1/s * 1e-6} = 0$$

Which can be rewritten as

$$\frac{V_o(s)}{V_i(s)} = 1.5 * \frac{s + (20/3)}{s + 5}$$